

RC Circuits

Text section 28.4


Practice: Chapter 28,

Objective Question 7

Conceptual Question 6

Problems 37, 41, 43, 63

Discussion

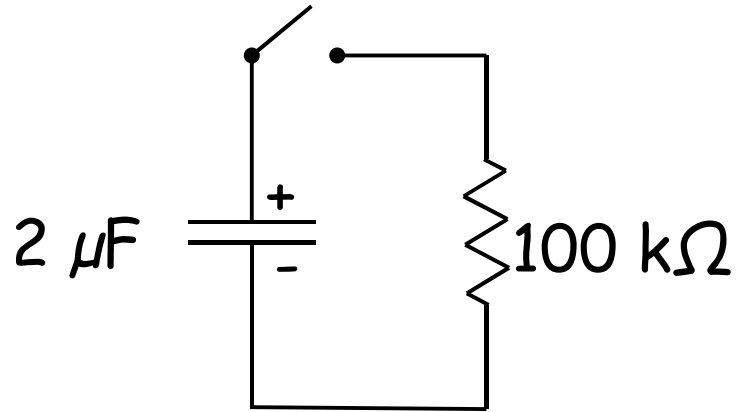

The capacitor has an initial charge of $20 \mu\text{C}$.

- The switch is now closed : What is the initial current through the resistor?
- How long would it take for all the charge to leak off if the current stayed constant?

Result:

time = resistance \times capacitance
(the units work out to seconds).


Actually, the current is not constant; as the charge decreases, the voltage decreases, so the current decreases, so charge decreases more and more slowly ...

Even so, (resistance) \times (capacitance) is a good first estimate of the time.

Quiz


The capacitor has zero initial charge. What is the battery current immediately after the switch is closed?

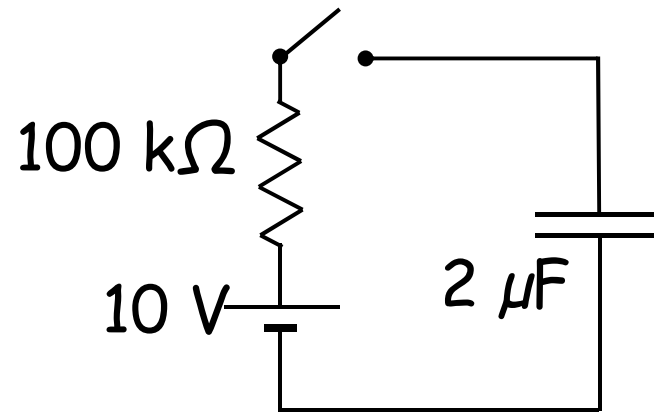- A) $20 \mu\text{A}$
- B) $5 \mu\text{A}$
- C) 50A
- D) $100 \mu\text{A}$
- E) 200mA




Quiz

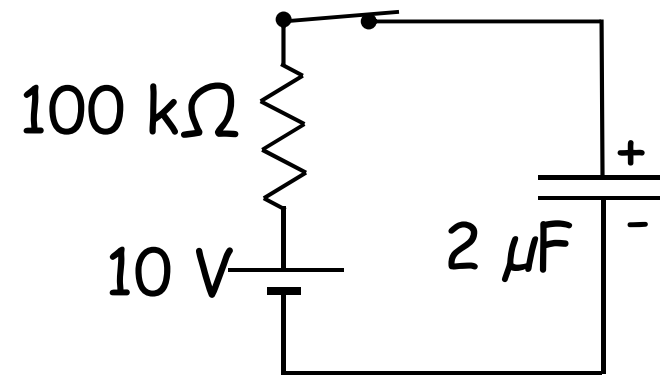The capacitor has zero initial charge. What will the charge on the capacitor be a long time after the switch is closed?




- A) $20 \mu\text{C}$
- B) $5 \mu\text{C}$
- C) 2 C
- D) zero
- E) It will increase without limit

Demonstration

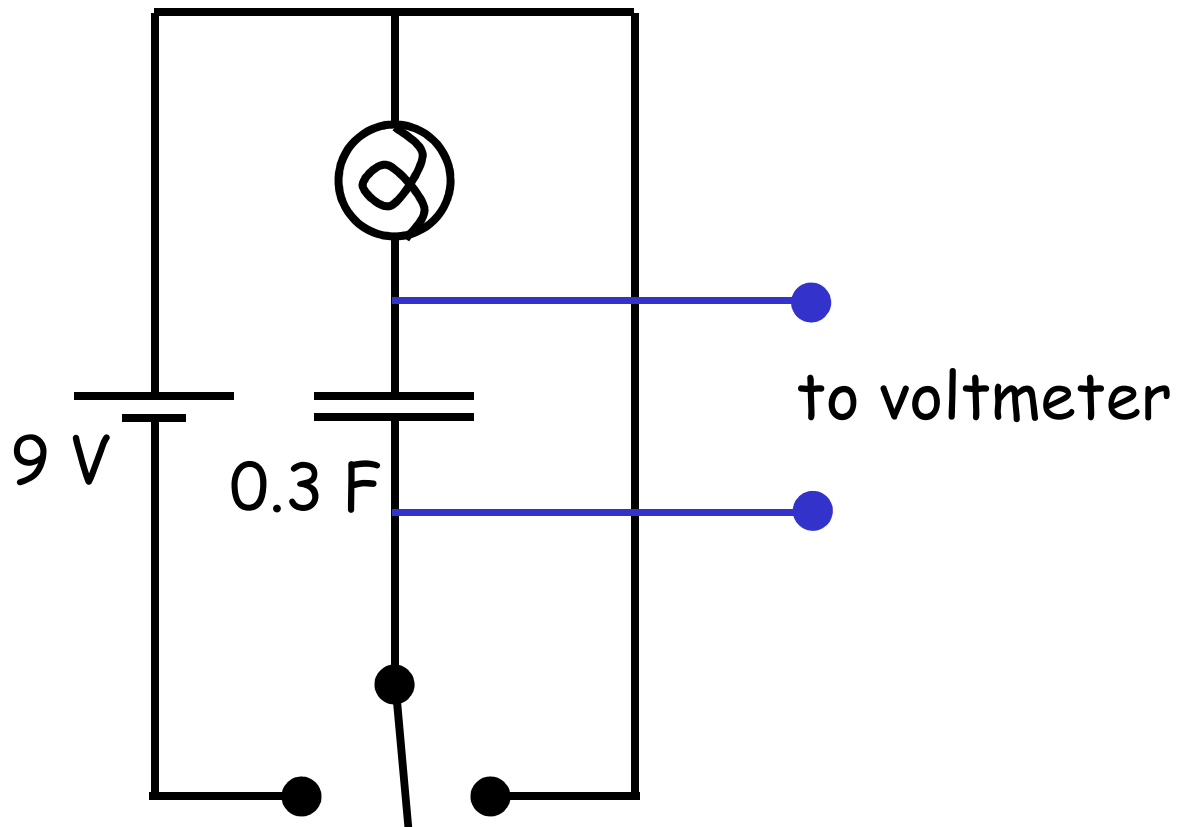

Discharging a Capacitor

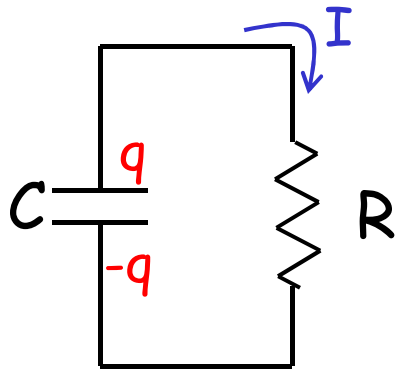

Given: R , C , q_0 (initial charge)


Find: $q(t)$ and $I(t)$

1) $\frac{q}{C} - IR = 0$ *(Kirchhoff's Loop Rule)*

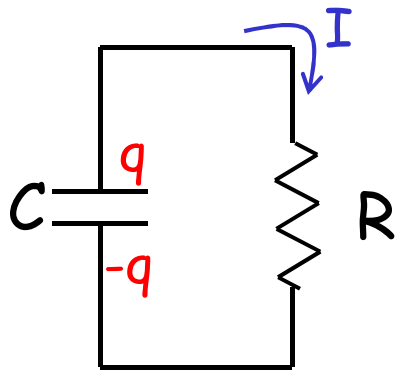2) $I = -\frac{dq}{dt}$ *(- sign because q decreases for $I > 0$)*

$$\Rightarrow \frac{q}{C} = -R \frac{dq}{dt}$$

$$\frac{dq}{dt} = -\frac{q}{RC} \quad \text{where } q = q(t), q(0) = q_0$$



$$\frac{dq}{dt} = -\frac{q}{RC} \quad \text{where } q = q(t)$$
$$q(0) = q_0$$

This is a **differential equation** for the **function** $q(t)$, subject to the **initial condition** $q(0) = q_0$.

We are looking for a function which is proportional to its own first derivative.

To solve: $dq = -\frac{q}{RC} dt$

$\Rightarrow \frac{dq}{q} = -\frac{1}{RC} dt$ *bring all the "q" variables to one side,
all the "t" variables to the other*

$\int_{q=q_0}^{q(t)} \frac{dq}{q} = \int_{t=0}^t \left(-\frac{1}{RC}\right) dt$ *then integrate each side*

$\ln q - \ln q_0 = -\frac{t}{RC}$

$\underbrace{\ln q - \ln q_0}_{\ln\left(\frac{q}{q_0}\right)}$

$\Rightarrow q(t) = q_0 e^{-\frac{t}{RC}}$


RC is called the "time constant" or "characteristic time" of the circuit.

Units: $1 \Omega \times 1 F = 1 \text{ second}$ (*Proof: exercise*)

Write τ ("tau") = RC , then

$$q(t) = q_0 e^{-\left(\frac{t}{\tau}\right)} \quad (\text{discharging}).$$

Discharging

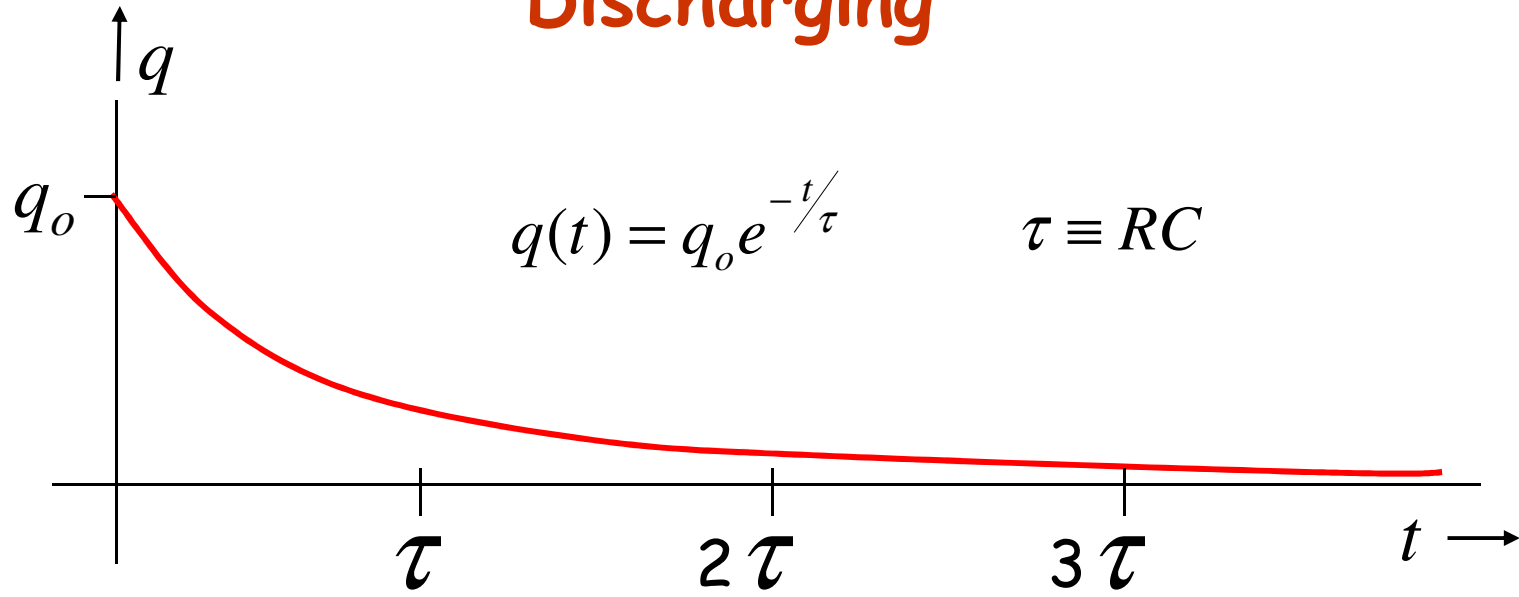

$$t = \tau, \quad q \approx 0.37 q_0$$

$$t = 2\tau, \quad q \approx 0.14 q_0$$

$$t = 3\tau, \quad q \approx 0.05 q_0$$


$$t \rightarrow \infty, \quad q \rightarrow 0$$

Quiz

A capacitor is charged up to 18 volts, and then connected across a resistor. After 10 seconds, the capacitor voltage has fallen to 12 volts. What will the voltage be after another 10 seconds (20 seconds total)?

- A) 0
- B) 6V
- C) 8V
- D) 9V
- E) 10V

Charging

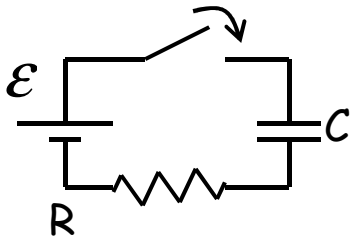

C is initially uncharged, and the switch is closed at $t=0$. After a long time, the capacitor has charge Q_f .


Then, $q(t) = Q_f \left(1 - e^{-t/\tau} \right)$ where $\tau = RC$.

Question: What is Q_f equal to?

Charging

$$q(t) = Q_f \left(1 - e^{-t/\tau} \right)$$

$$\tau = RC$$

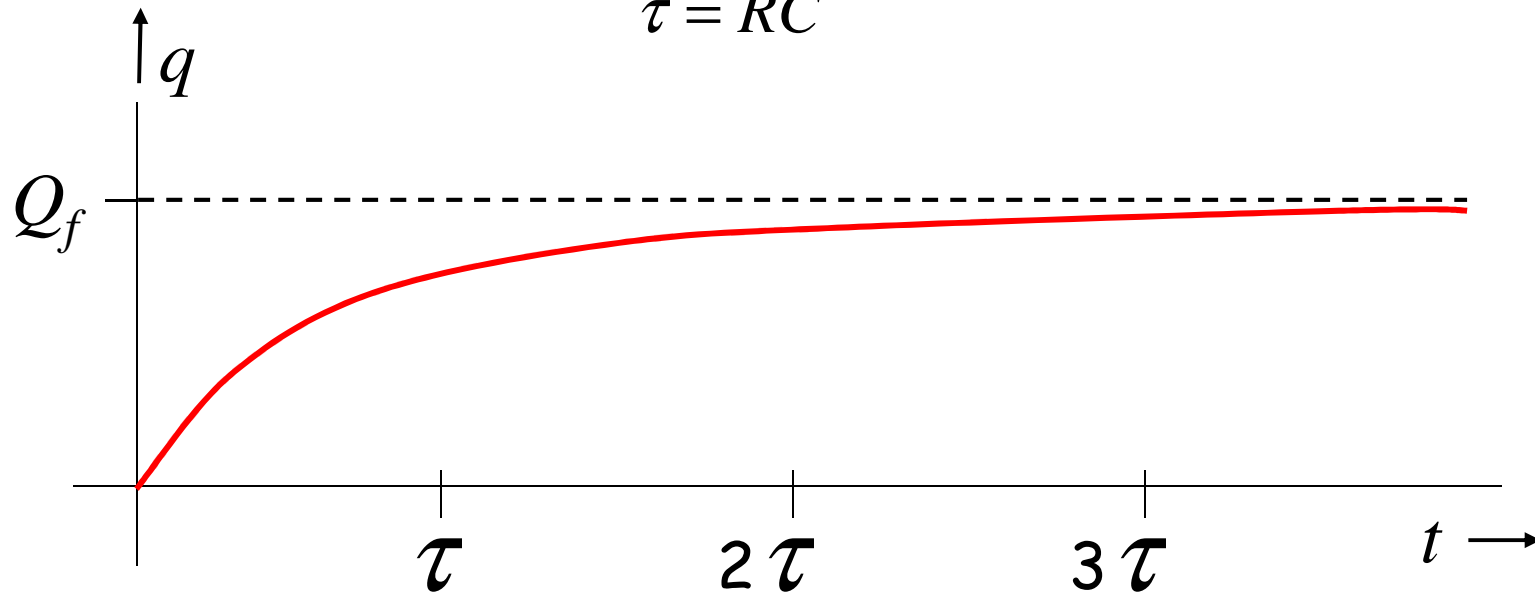

$$t = 0, \quad q = 0$$


$$t = RC, \quad q \approx 0.63 Q_f$$

$$t = 2 RC, \quad q \approx 0.86 Q_f$$


$$t = 3 RC, \quad q \approx 0.95 Q_f$$

etc.


Quiz

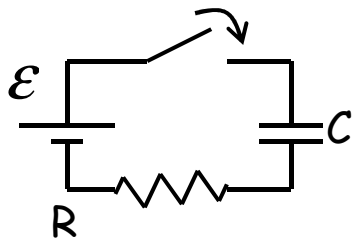

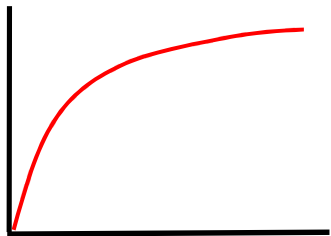
C is initially uncharged, and the switch is closed at $t=0$. Which graph below shows the current as a function of time?



A)

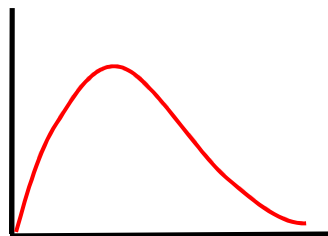

B)

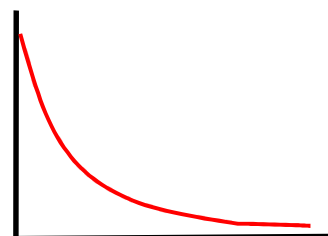


C)



D)

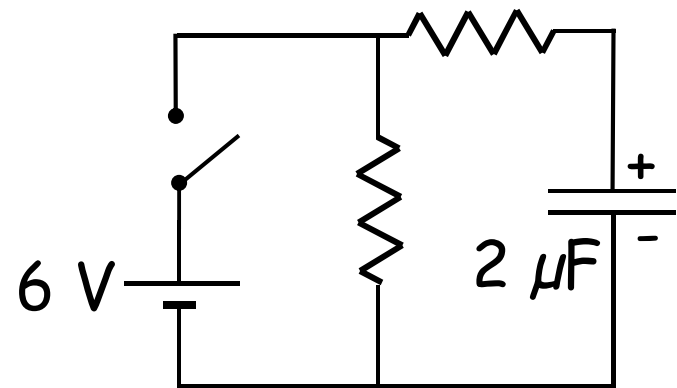
Exercise

The capacitor has zero initial charge, and each resistor is $200\text{ k}\Omega$. Find the charge on the capacitor, and the current through each component, as functions of time.



More Difficult Exercise

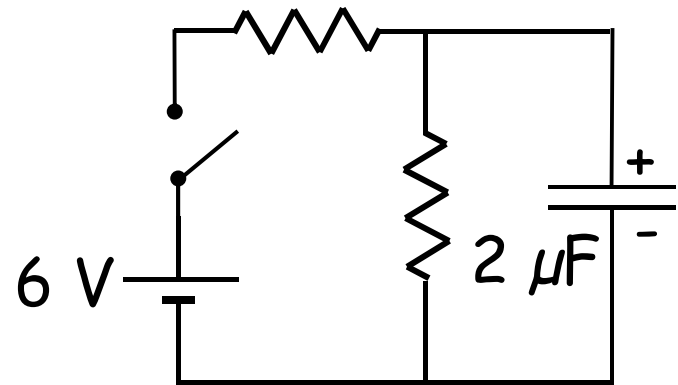The capacitor has zero initial charge, and each resistor is $200\text{ k}\Omega$. Find the charge on the capacitor, and the current through each component, as functions of time.



"RC" Circuits

- a capacitor takes *time* to charge or discharge through a resistor
- "time constant" or "characteristic time"

$$\tau = RC$$

$$(1 \text{ ohm}) \times (1 \text{ farad}) = 1 \text{ second}$$